

MOTION DETECTOR KIT

MODEL AK-510



Assembly and Instruction Manual

PARTS LIST

RESISTORS

QTY	SYMBOL	DESCRIPTION	COLOR CODE	PART #
□ 1	R16	300Ω 5% 1/4W	orange-black-brown-gold	133000
□ 1	R15	5.6kΩ 5% 1/4W	green-blue-red-gold	145600
□ 1	R5	39kΩ 5% 1/4W	orange-white-orange-gold	153900
□ 4	R1, 2, 8, 9	47kΩ 5% 1/4W	yellow-violet-orange-gold	154700
□ 1	R3	75kΩ 5% 1/4W	violet-green-orange-gold	157500
□ 1	R14	270kΩ 5% 1/4W	red-violet-yellow-gold	162700
□ 2	R11, R12	300kΩ 5% 1/4W	orange-black-yellow-gold	163000
□ 1	R10	510kΩ 5% 1/4W	green-brown-yellow-gold	165100
□ 1	R6	620kΩ 5% 1/4W	blue-red-yellow-gold	166200
□ 1	R7	1.2MΩ 5% 1/4W	brown-red-green-gold	171200
□ 1	R4	1.6MΩ 5% 1/4W	brown-blue-green-gold	171600
□ 1	R13	1.8MΩ 5% 1/4W	brown-gray-green-gold	171800

CAPACITORS

QTY	SYMBOL	VALUE	DESCRIPTION	PART #
□ 1	C8	500pF (501)	Discap	225080
□ 1	C9	.01μF (103)	Discap	241031
□ 2	C2, C3	10μF 25V	Electrolytic (Lytic)	271045
□ 2	C4, C5	22μF 25V	Electrolytic (Lytic)	272245
□ 2	C1, C6	100μF 16V	Electrolytic (Lytic)	281044

SEMICONDUCTORS


QTY	SYMBOL	VALUE	DESCRIPTION	PART #
□ 1	D1	1N4148	Diode	314148
□ 1	Q1	MPSA18	Transistor NPN	320018
□ 1	IC1	LM324	Integrated Circuit	330324
□ 1	IC2	HT2810	Integrated Circuit	332810
□ 1	IC3	78L05	Integrated Circuit	338L05
□ 1	S1	LHI-954 / KDS245	Infrared Detector	350954

MISCELLANEOUS

QTY	DESCRIPTION	PART #	QTY	DESCRIPTION	PART #
□ 1	PC Board	517019	□ 1	Battery Cover	626005
□ 1	Speaker w/ Wires	520813	□ 2	Screw #4 x 1/4"	642430
□ 1	Switch Key	540105	□ 2	Screw #4 x 5/8"	643450
□ 1	SW1 - Slide Switch	541007	□ 2	Washer #4 (Fiber)	645404
□ 1	Battery Snap	590098	□ 1	Socket IC 8-Pin	664008
□ 1	Front Cover	623104	□ 1	Socket IC 14-Pin	664014
□ 1	Back Cover	623202	□ 1	Solder Tube	9ST4
□ 1	Mounting Bracket	626004			

PARTS IDENTIFICATION

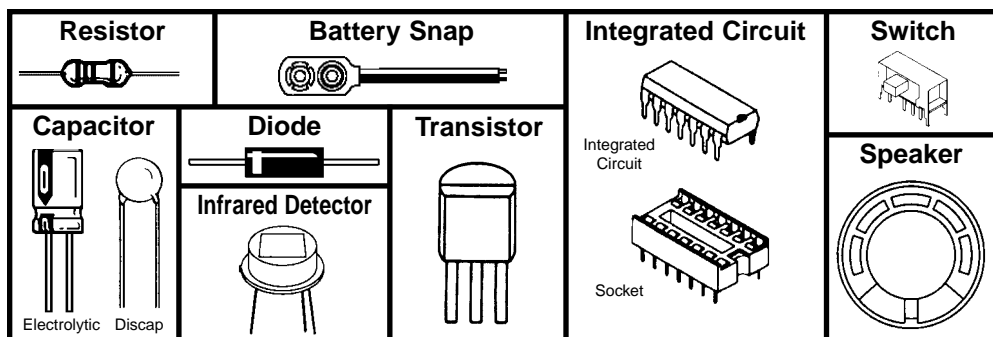
Note: The text printed on the LHI-954 Infrared Detector is the date code.



IDENTIFYING RESISTOR VALUES

Use the following information as a guide in properly identifying the value of resistors.

BAND 1 1st Digit		BAND 2 2nd Digit		Multiplier		Resistance Tolerance	
Color	Digit	Color	Digit	Color	Multiplier	Color	Tolerance
Black	0	Black	0	Black	1	Silver	$\pm 10\%$
Brown	1	Brown	1	Brown	10	Gold	$\pm 5\%$
Red	2	Red	2	Red	100	Brown	$\pm 1\%$
Orange	3	Orange	3	Orange	1,000	Red	$\pm 2\%$
Yellow	4	Yellow	4	Yellow	10,000	Orange	$\pm 3\%$
Green	5	Green	5	Green	100,000	Green	$\pm .5\%$
Blue	6	Blue	6	Blue	1,000,000	Blue	$\pm .25\%$
Violet	7	Violet	7	Silver	0.01	Violet	$\pm .1\%$
Gray	8	Gray	8	Gold	0.1		
White	9	White	9				

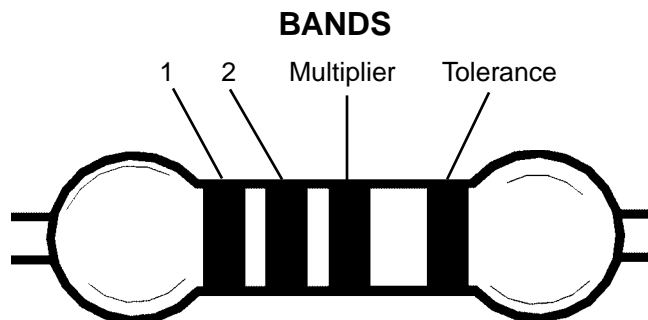


IDENTIFYING CAPACITOR VALUES

Capacitors will be identified by their capacitance value in pF (picofarads) or μF (microfarads). Most capacitors will have their actual value printed on them. Some capacitors may have their value printed in the following manner. The maximum operating voltage may also be printed on the capacitor.

Multiplier	For the No.	0	1	2	3	4	5	8	9
		Multiply By	1	10	100	1k	10k	100k	.01

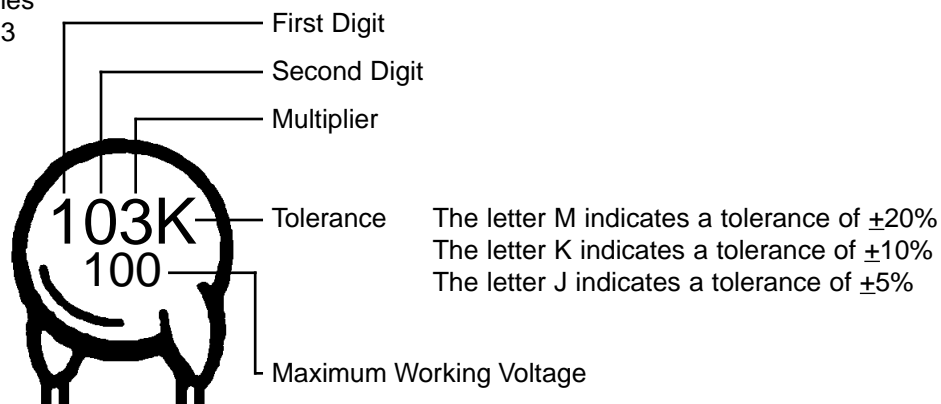Note: The letter "R" may be used at times to signify a decimal point; as in 3R3 = 3.3



The value is $10 \times 1,000 = 10,000\text{pF}$ or $.01\mu\text{F}$ 100V

CONSTRUCTION

Introduction

The most important factor in assembling your AK-510 Motion Detector Kit is good soldering techniques. Using the proper soldering iron is of prime importance. A small pencil type soldering iron of 25 - 40 watts is recommended. **The tip of the iron must be kept clean at all times and well tinned.**

Safety Procedures

- Wear eye protection when soldering.
- Locate soldering iron in an area where you do not have to go around it or reach over it.
- **Do not hold solder in your mouth.** Solder contains lead and is a toxic substance. Wash your hands thoroughly after handling solder.
- Be sure that there is adequate ventilation present.

Assemble Components

In all of the following assembly steps, the components must be installed on the top side of the PC board unless otherwise indicated. The top legend shows where each component goes. The leads pass through the corresponding holes in the board and are soldered on the foil side.


Use only rosin core solder of 63/37 alloy.

DO NOT USE ACID CORE SOLDER!


What Good Soldering Looks Like

A good solder connection should be bright, shiny, smooth, and uniformly flowed over all surfaces.

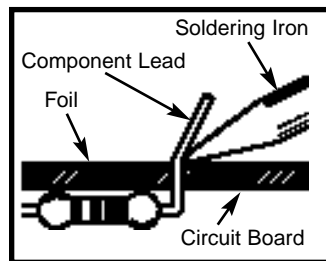
1. Solder all components from the copper foil side only. Push the soldering iron tip against both the lead and the circuit board foil.



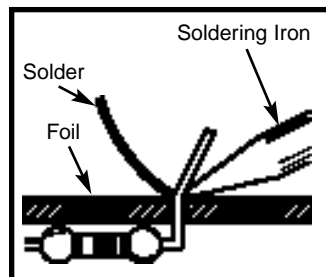2. Apply a small amount of solder to the iron tip. This allows the heat to leave the iron and onto the foil. Immediately apply solder to the opposite side of the connection, away from the iron. Allow the heated component and the circuit foil to melt the solder.



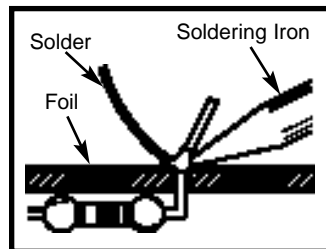3. Allow the solder to flow around the connection. Then, remove the solder and the iron and let the connection cool. The solder should have flowed smoothly and not lump around the wire lead.




4. Here is what a good solder connection looks like.




Types of Poor Soldering Connections

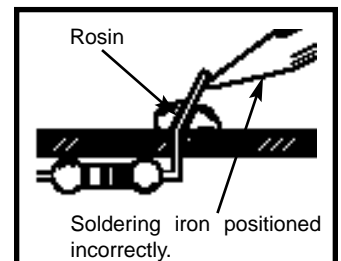
1. **Insufficient heat** - the solder will not flow onto the lead as shown.



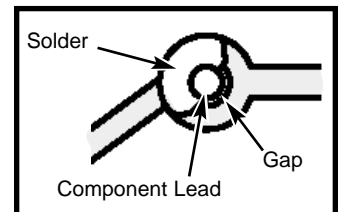
2. **Insufficient solder** - let the solder flow over the connection until it is covered. Use just enough solder to cover the connection.



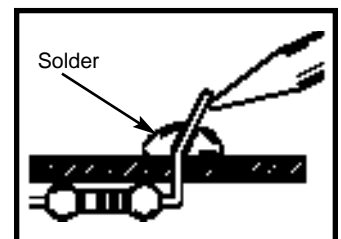3. **Excessive solder** - could make connections that you did not intend to between adjacent foil areas or terminals.




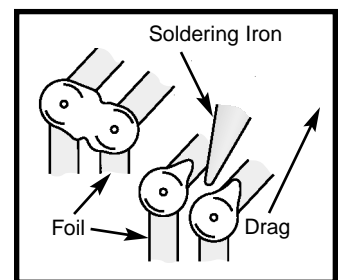4. **Solder bridges** - occur when solder runs between circuit paths and creates a short circuit. This is usually caused by using too much solder. To correct this, simply drag your soldering iron across the solder bridge as shown.



INTRODUCTION

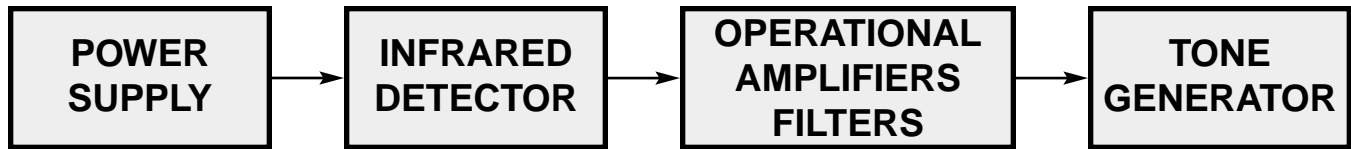The AK-510 is an infrared motion detector kit. The objective of the kit is to teach the operations of the four sections that make up the kit. The four sections are shown in the block diagram below.



There are many applications for the use of the detector. The most common is in the alarm system industry. Some of the new applications are automatic door openers, light switches in hallways, stairways and areas that increase safety for the public. Further applications can be seen in automatic production lines, switching of sanitary facilities, monitors and intercoms. With the ease of installation and the low susceptibility to interference from other forms of radiation, such as heaters or windows, the IR detectors are ideal devices.

POWER SUPPLY (see page 16)

A 9 volt battery is used to supply the DC voltage to the circuit. The battery voltage must be regulated (held as close as possible) to 5 volts. This is done by circuits called voltage regulators.

In order to see how this is accomplished, let's consider the analogy of a water tower. Voltage in electronics can be compared to water pressure in a water system. When water is pumped into a water tower, the pressure at the bottom of the tower can be quite high. In order to keep a constant pressure in the water pipes that go to the houses, the pressure must be lowered and held constant.

Consider the system shown in Figure 1. As people draw water into their homes, the pressure on the low pressure side of the valve drops. The spring pulls the valve arm inside the pipe up along opening the valve and allowing more water into the pipe. As the pressure on the low pressure side increases, it pushes the valve arm inside the pipe down closing the valve and stretching the spring. By increasing the spring pressure on the arm, the pressure on the low side will have to increase to close the valve. The force or pressure of the spring, therefore sets the value of the pressure on the low pressure side of the system. The force of the spring is called the reference pressure.

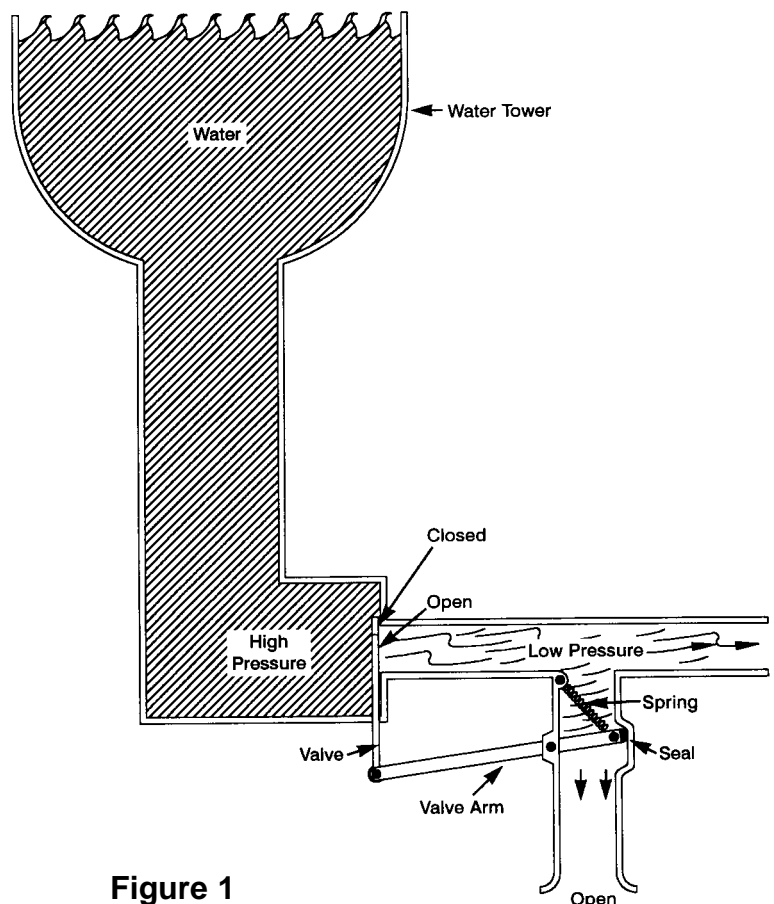



Figure 1

Voltage in electronics is the analogy to pressure in water pipes. A voltage greater than 7V is applied to the input of high voltage side of the regulator. A fixed reference voltage inside the regulator will set the low voltage output at 5 volts +5%. This is accomplished in a manner very similar to our water tower analogy. The output voltage is filtered or made smooth (no ripples) by capacitor C6 (100 μ F).

INFRARED DETECTOR

Infrared light was first discovered back in 1801 by W. Herschel. Infrared is a form of radiated energy in which the wavelength is longer than the wavelength of visible light. A wavelength can best be understood by the physical analogy shown in Figure 2.

If you were standing at the beach watching the waves come in to shore, you would be able to see the peaks of each wave as they approached. If you could measure the distance from one peak to the next, you would know the "Wavelength" of those waves. We will use the eleventh letter of the Greek alphabet " λ " (lambda) to represent the distance between valleys to determine the length of the wave (see Figure 2). A wavelength can be defined as the distance between any two exactly equal points on identically repeating waves.

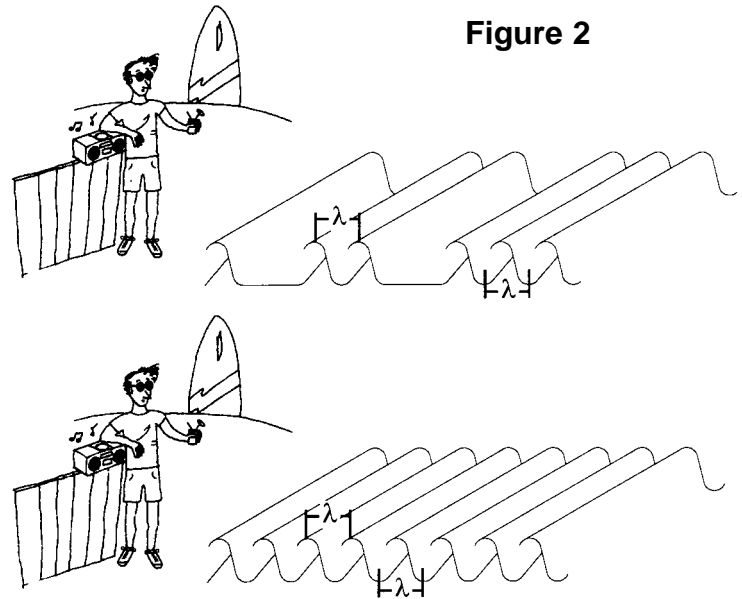

What would happen if we reduced the distance between the peaks to 1/2 the original distance. Would it not be true, the peaks would strike the shore twice as often as before? The frequency of the peaks reaching the shore would be twice that of the longer wave. For people who like big words, we would say "Frequency is inversely proportional to the wavelength". In simple words, "If the wavelength goes up, the frequency goes down and if the wavelength goes down, the frequency goes up". The mathematics of waves applies also to the radiation of light. It is common practice, therefore, to talk about light as lightwaves. The wavelength of infrared light ranges from .78 micrometers (μm) to 100 (μm). A micrometer is one millionth of a meter.

Infrared can be thought of as heat radiation because the radiant energy is transformed into heat when it strikes a solid surface. All solid bodies at a temperature above absolute zero emit thermal radiation. As a body's temperature rises, the shorter the resulting wavelengths become. The human body's maximum thermal radiation is between $9\mu\text{m}$ and $10\mu\text{m}$ in the infrared stage. Motion can be detected by special elements which are highly sensitive in the infrared range. Such devices are called Pyroelectric Infrared Detectors.

PYROELECTRIC EFFECT

When certain materials change temperature, they produce electricity. A Pyroelectric crystal is an example of such a material. If a Pyroelectric crystal has been at the same temperature for a period of time, there will be no voltage across its electrodes. When the crystal temperature changes, a voltage is produced at the electrodes of the crystal element. This type of crystal is used in this motion detector kit inside the infrared (IR) detector.

INTERNAL DESIGN

The IR detector contains two crystals connected with each other in opposite polarity and with a 1 millimeter (mm) optical spacing. These two crystals are located behind an optical filter or lens (see Figure 3). The output power of the crystals is very low. A special device called the Field Effect Transistor (FET) is used to increase the power output. The FET can be compared to water pipes as shown in Figure 4. The center of a small section of pipe is made of thin, flexible rubber surrounded by water from a third pipe called the gate. When pressure (voltage) is applied to the gate, the rubber tube closes and pinches off the flow of water (current) from source to drain. In a similar manner, as infrared radiation is detected, the crystals produce a voltage at the gate

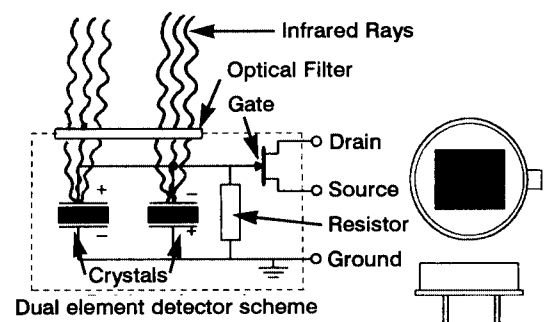


Figure 3

of the FET. This causes a change in current from the drain to source. Very little power is required at the gate to control the larger current flow from source to drain. The benefits of this type of detector are low radio interference, low noise, specially suited response. The IR detector is sealed in a metal housing to prevent electromagnetic interference and to keep them clean.

FIELD OF VIEW

Detectors are available with different fields of view, depending on the application. The maximum distance and total angle of view are important specifications needed in choosing a motion detector. The LHI-954 field of view is shown in Figure 5.

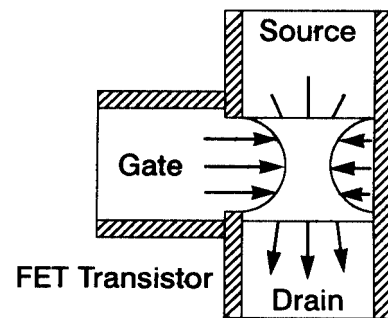


Figure 4

CIRCUIT DESCRIPTION (see page 16)

The IR Section contains only a few components, R1, R2, C1 and the PIR sensor. As motion is detected, the IR detector will produce a voltage at the gate of the FET allowing current to flow from the drain to source, causing the voltage at the input of U1 (pin 13) to change, thus changing the output at pin 14. Resistors R1 and R2 limit the amount of current flow through the FET.

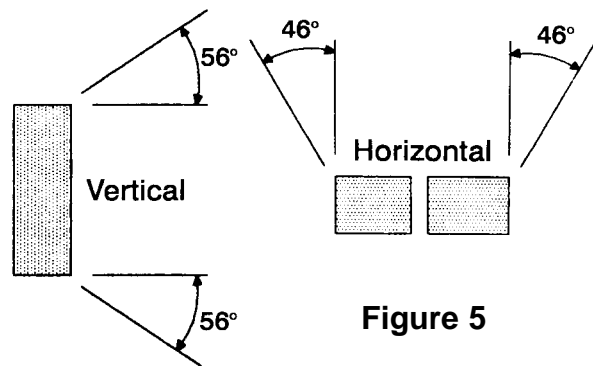


Figure 5

OPERATIONAL AMPLIFIERS / FILTERS

An amplifier is a device that uses a small amount of power to control a larger amount of power. Just like a small amount of power on the valve arm of Figure 1 controlled the water pressure in the pipes going to the houses. The amplifier does not create power (it was already there in the water tower) but it controls the power from a source.

In electronics, amplifiers are composed of devices called transistors, resistors, and capacitors. The number of these components used and the way they are assembled determines the characteristics of the amplifier. An amplifier that can perform many mathematical operations such as adding, subtracting, or multiplying voltages is called an Operational Amplifier or Op-Amp.

The characteristics of an ideal op-amp are the following:

- A. infinite voltage gain (no voltage at all on the input controls, large voltage on the output).
- B. infinite bandwidth (no matter how fast the input changes, the output will change just as fast).
- C. infinite input impedance (no power required at input to change output).
- D. zero output impedance (the output can deliver an infinite amount of power).

Obviously, in the real world these conditions can never be met, but for mathematical purposes they are assumed in designing electronic circuits with op-amps.

The op-amp has two input terminals, inverting input (--) and non-inverting input (+), and one output terminal. Figure 6 shows the standard op-amp symbol. The two input terminals are labeled 2 and 3, and the output is 1. Most op-amps operate with two DC power supplies, +V_{CC} and -V_{EE} connect to pins 11 and 4 respectively. Since a single power supply is used in the kit, -V_{EE} (pin 4) is tied to ground. The op-amp multiplies the difference between the voltage signals applied at its two input terminals (V₃-V₂) times the gain of the amplifier (A). A x (V₃-V₂) appears at the output terminal as shown in Figure 7.

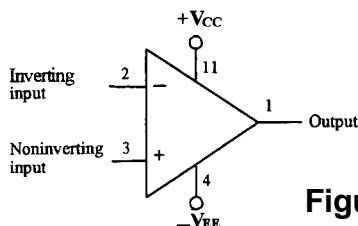


Figure 6

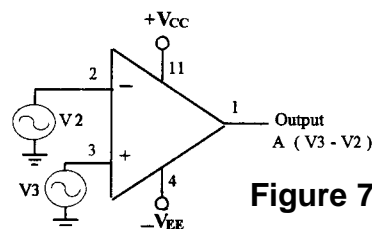


Figure 7

NEGATIVE FEEDBACK

The open loop gain (or maximum gain) of a typical op-amp is very high (usually greater than 100,000), enabling a very small input voltage to drive the op-amp output to its extremes. To prevent this, a resistor is connected between the output and inverting input terminals allowing a portion of the output signal to be brought back and cancel part of the input (Figure 8). This process is called Negative Feedback. The signal being fed back is out of phase with the input and thus subtracts from the input signal. If the resistor was connected between the non-inverting input and output terminals, it would be called Positive Feedback. The closed loop gain (or gain after feedback) from the input V_i to the output terminal depends on the ratio of R_2 to R_1 .

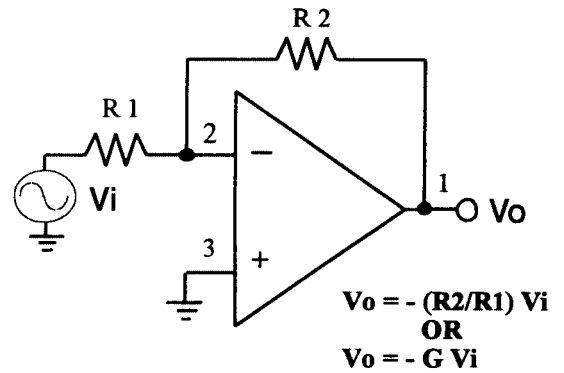


Figure 8

For example, if $R_2 = 100$ and $R_1 = 10$, the gain (G) = $R_2/R_1 = 100/10 = 10$. Thus, the output voltage V_o would be equal to $-10(V_i)$. The (-) sign indicates that the output and input voltages are of opposite polarity.

VOLTAGE COMPARATOR

Operational amplifiers can be used to compare the amplitude of one voltage with another. As a comparator, its function is to determine when an input voltage exceeds a certain level. When used as a comparator, the op-amp is used without feedback and at maximum gain. One input is set to a reference voltage and the other tied to the input voltage.

FILTERS

LOW PASS FILTER

A low pass filter attenuates (decreases) all signals above a certain frequency and passes frequencies below that frequency. An example of a low pass filter is a simple RC network as shown in Figure 9. Low frequencies are passed unharmed. As the frequency rises the output is reduced (see Figure 10).

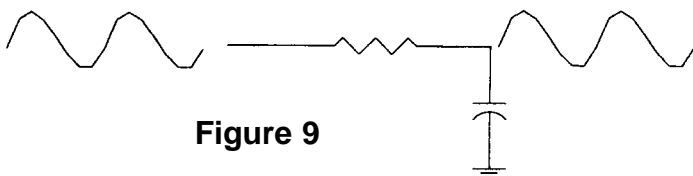


Figure 9

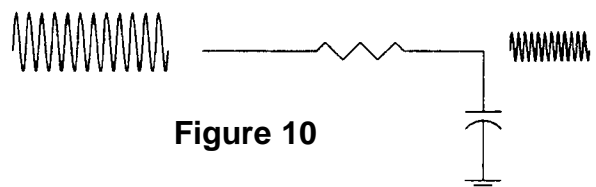


Figure 10

HIGH PASS FILTER

The high pass filter attenuates frequencies below a certain frequency and passes frequencies above that frequency. An example of a high pass filter is a simple RC network as shown in Figure 11. Low frequencies are reduced when passed through the filter while high are passed unharmed (see Figure 12).

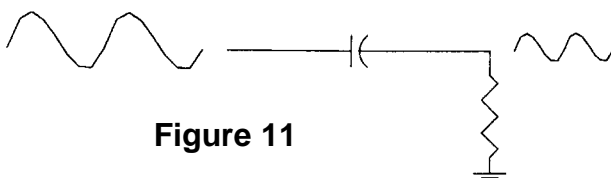


Figure 11

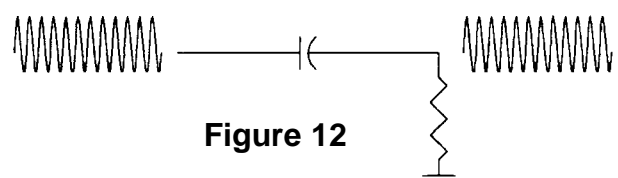


Figure 12

BAND PASS FILTER

The combination of a low and high pass filter create what is called a Band Pass Filter. The frequencies passed by each filter overlap and create a bandwidth (range), passing all signals within the bandwidth and reducing all others. Figure 13 illustrates the general band-pass response curve. A critical frequency is defined as the point where the voltage is reduced to .707 (the square root of 1/2 is used because it represents the point where power has been reduced to 1/2). The bandwidth can be defined as the difference between the upper critical frequency (f_{c2}) and the lower critical frequency f_{c1} ($BW = f_{c2} - f_{c1}$). The selectivity (or Quality) of a band-pass filter is expressed as the “Q” of the filter. It is the ratio of the center (or Resonant) frequency to the bandwidth ($Q = f_r/BW$). A filter with a higher value of Q has a narrower bandwidth, thus passing fewer frequencies than one with a lower value. Bandpass filters can be classified as either a narrow-band ($Q \geq 10$) or a wide-band ($Q < 10$).

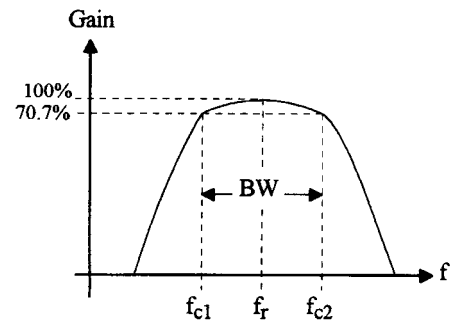


Figure 13

CIRCUIT DESCRIPTION (See page 16)

The op-amp IC1D shapes the frequency response to amplify those frequencies produced when motion is detected and rejects all others, such as those due to noise or slow temperature changes. Frequencies above 20Hz and below 1Hz are beyond the bandwidth of the circuit and thus are rejected. The output at pin 14 is about 1.6V when no motion is detected. As motion is detected, the voltage at the output will change and trigger either IC1C or IC1B.

The op-amps IC1A, IC1B and IC1C are configured as voltage comparators. In the ready state, the output of IC1A is high and IC1B and IC1C are low. When IC1D outputs a voltage lower than 1.41V, it will force pin 2 of IC1 high. When IC1D outputs a voltage higher than 1.67V, it forces pin 8 and pin 2 of IC1 to go high. A high in with one of these cases causes the output to go low and allows C9 to discharge through IC1A. The discharging of C9 will pull pin 6 of IC2 low and trigger the sound generator.

SOUND GENERATOR

The circuit uses an HT-2810 sound generator IC. Figure 14 shows the internal design of the IC. As the Key Input is brought low, the Oscillator, Speed Generator, Tone Generator, Noise Generator and Envelope Sections are all enabled. The Oscillator Section begins to oscillate at a frequency determined by the voltage across pins 7 and 8. This frequency is then divided down and applied to the Speed Generator. The Speed Generator controls the frequency of the output as it is applied to the output driver.

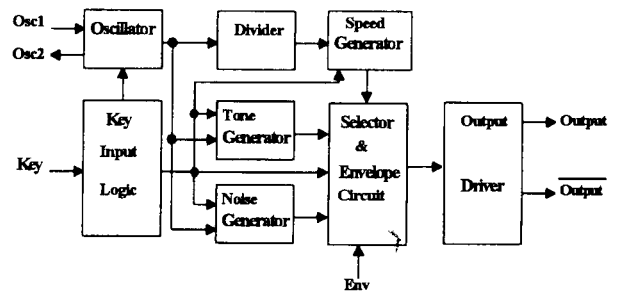


Figure 14

CIRCUIT DESCRIPTION (see page 16)

Switch SW1 has three positions: LOW / OFF / HIGH. In the LOW mode, the IC outputs a series of pulses at 892Hz, then a series of pulses at 714Hz to get the ding-dong sound effect. The HIGH mode outputs a series of pulses at 1kHz and a series of pulses at 961Hz. The amplitude of the output of pin 3 is ramped down (see Figure 15) by placing capacitor C5 from pin 4 to ground. As the voltage from the output decreases, it causes the speaker's sound to decrease. This contributes to the ding-dong effect.

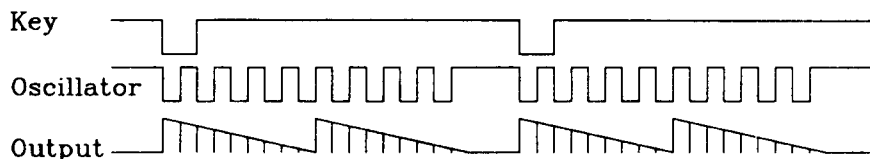


Figure 15

ASSEMBLE COMPONENTS TO THE PC BOARD

- R2 - 47kΩ 5% 1/4W Resistor (yellow-violet-orange-gold)
- C2 - 10μF 25V Electrolytic (see Figure D)
- C4 - 22μF 25V Electrolytic (see Figure D)
- R5 - 39kΩ 5% 1/4W Resistor (orange-white-orange-gold)
- R3 - 75kΩ 5% 1/4W Resistor (violet-green-orange-gold)
- C8 - 500pF (501) Discap
- D1 - 1N4148 Diode (see Figure A)
- R4 - 1.6MΩ 5% 1/4W Resistor (brown-blue-green-gold) (See Note)
- R6 - 620kΩ 5% 1/4W Resistor (blue-red-yellow-gold) (See Note)
- R9 - 47kΩ 5% 1/4W Resistor (yellow-violet-orange-gold)
- 14-pin IC Socket
IC1 - LM324 Integrated Circuit (see Figure C)
- R12 - 300kΩ 5% 1/4W Resistor (orange-black-yellow-gold)
- R11 - 300kΩ 5% 1/4W Resistor (orange-black-yellow-gold)
- R10 - 510kΩ 5% 1/4W Resistor (green-brown-yellow-gold)
- C9 - .01μF (103) Discap
- C6 - 100μF 16V Electrolytic (see Figure D)
- IC3 - 78L05 Integrated Circuit (see Figure B)
- D2 - Use a Jumper Wire in place of the diode.
- C5 - 22μF 25V Electrolytic (see Figure D)



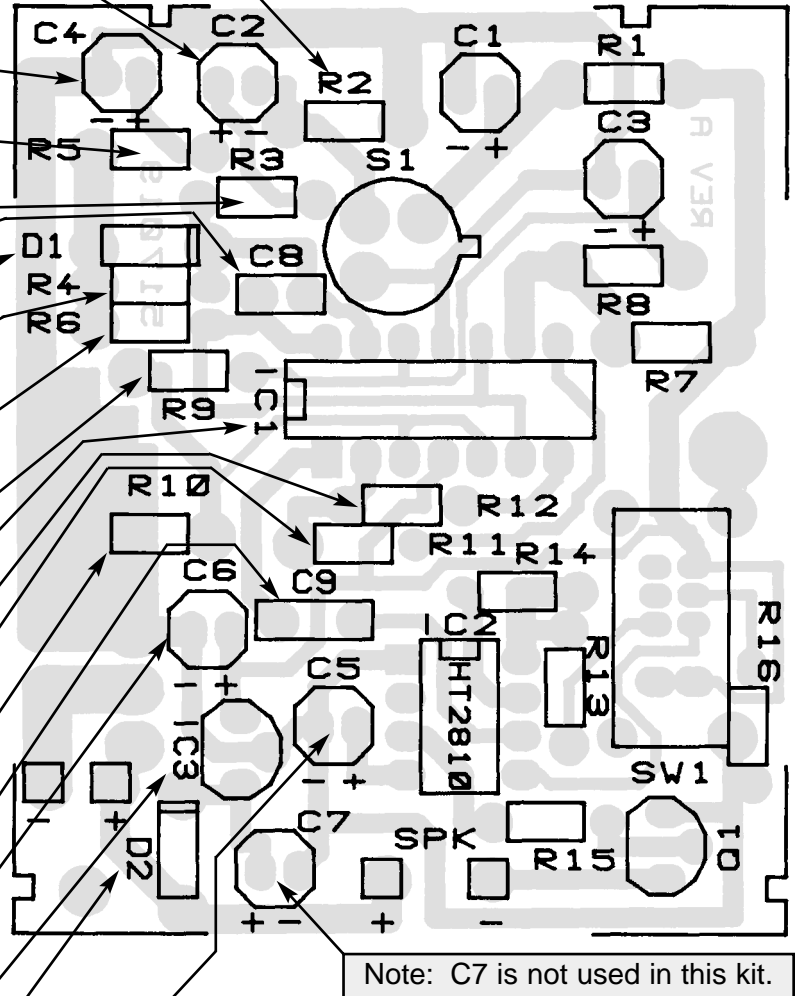


Figure A

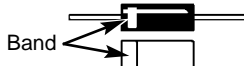

Diodes have polarity. Be sure to mount them with the band going in the same direction as marked on the PC board.

Figure B

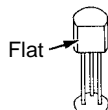

Mount the device with the flat side in the same direction as shown on the PC board. Solder and cut off the excess leads.

Figure C

Align the socket notch (if any) with the notch marked on the PC board. Solder the socket to the PC board. Insert the IC into the socket with the notch as shown below.


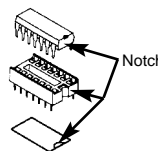


Figure D

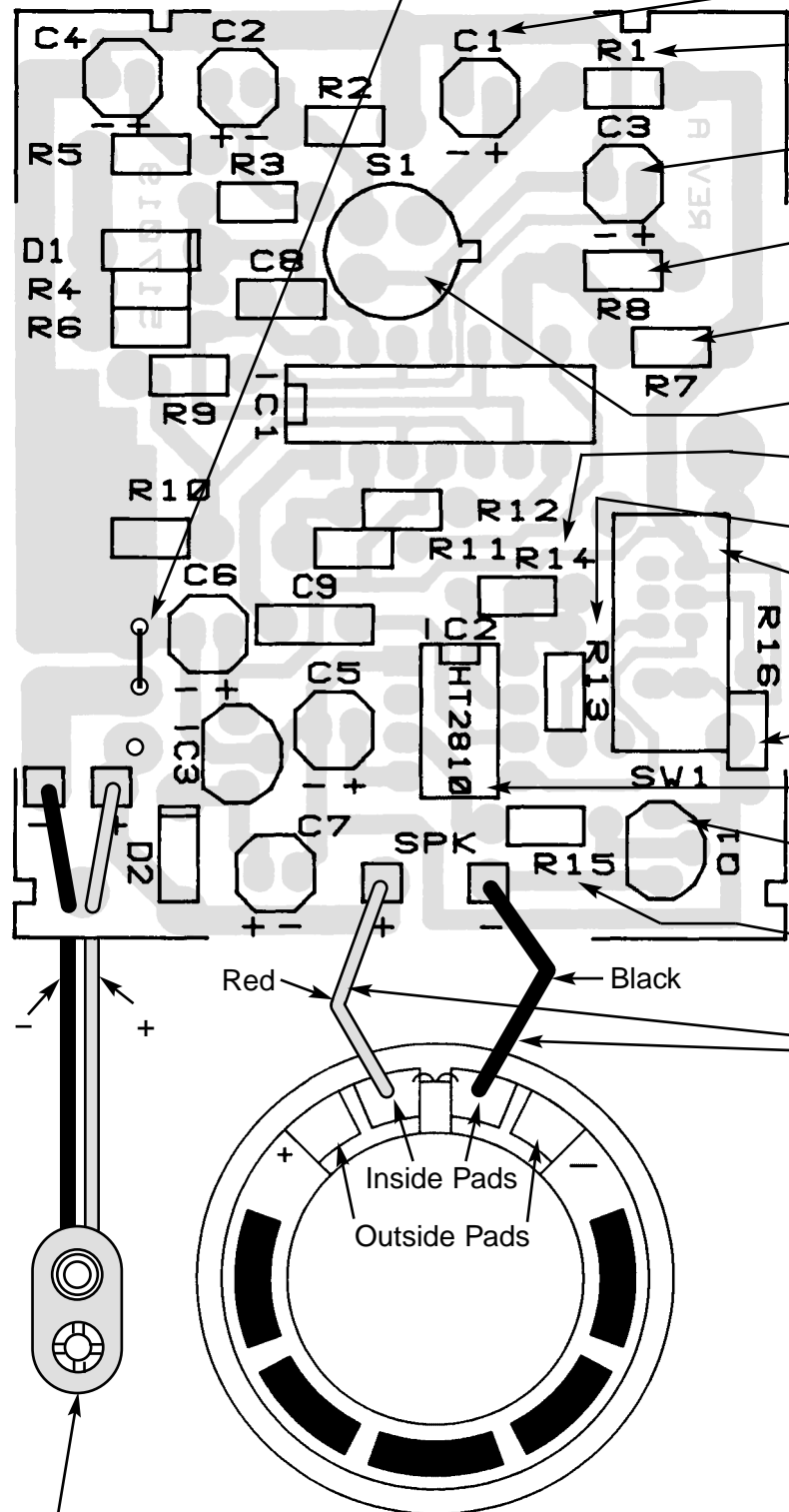These capacitors are polarized. Be sure to mount them with the "+" lead in the correct hole as marked on the PC board.



ASSEMBLE COMPONENTS (CONTINUED)



- Jumper Wire (see Figure E)
 - C1 - 100 μ F 16V Electrolytic (see Figure D)
 - R1 - 47k Ω 5% 1/4W Resistor (yellow-violet-orange-gold)
 - C3 - 10 μ F 25V Electrolytic (see Figure D)
 - R8 - 47k Ω 5% 1/4W Resistor (yellow-violet-orange-gold)
 - R7 - 1.2M Ω 5% 1/4W Resistor (brown-red-green-gold)
 - S1 - LHI-954 Infrared Detector
Mount with tab in the same direction as marked on the PC board (see note below).
 - R14 - 270k Ω 5% 1/4W Res. (red-violet-yellow-gold)
 - R13 - 1.8M Ω 5% 1/4W Resistor (brown-gray-green-gold)
 - SW1 - Slide Switch
 - R16 - 300 Ω 5% 1/4W Resistor (orange-black-brown-gold)
 - 8-pin IC Socket
IC2 - HT2810 Integrated Circuit (see Figure C)
 - Q1 - MPSA18 Transistor (see Figure B)
 - R15 - 5.6k Ω 5% 1/4W Resistor (green-blue-red-gold)
 - Speaker Wires - Solder the two wires to the PC board marked SPK +,-.
- Note:** If wires need resoldering;
 1. First apply a small amount of solder to the outside pad.
 2. Solder the speaker wire to the outside pads.
- CAUTION:** The internal speaker wires are soldered to the inside pads. **DO NOT** unsolder these wires.

B1 - Battery Snap
 Identify the battery snap B1. Insert the red and black wires through the hole from the copper side of the PC board. Insert the red wire into the (+) positive hole and the black wire into the (-) negative hole as shown above.

Note: The text printed on the LHI-954 Infrared Detector is the date code.

Figure E
 Use a discarded lead for a jumper wire.

FINAL ASSEMBLY

□ Step 1

Place the speaker into the front case as shown in Figure 16. Use two #4 x 1/4" screws and two #4 washers to secure it into place.

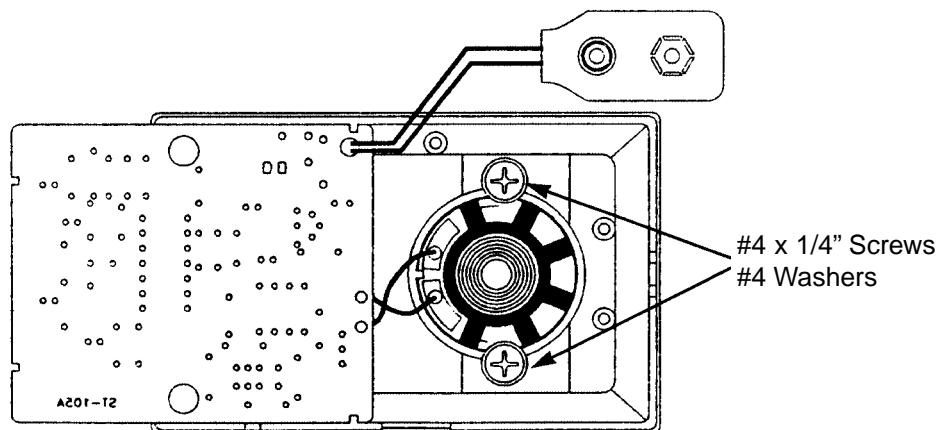


Figure 16

□ Step 2

Push the switch key onto the switch as shown in Figure 17. Make sure that the key-switch is sitting properly on the switch.

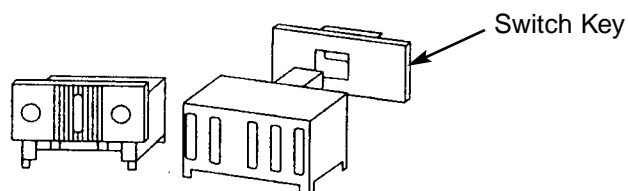


Figure 17

□ Step 3

Place the PC board into the front case as shown in Figure 18. Attach the back case to the front case with two #4 x 5/8" screws. **Note:** There is a small groove that the key switch fits into.

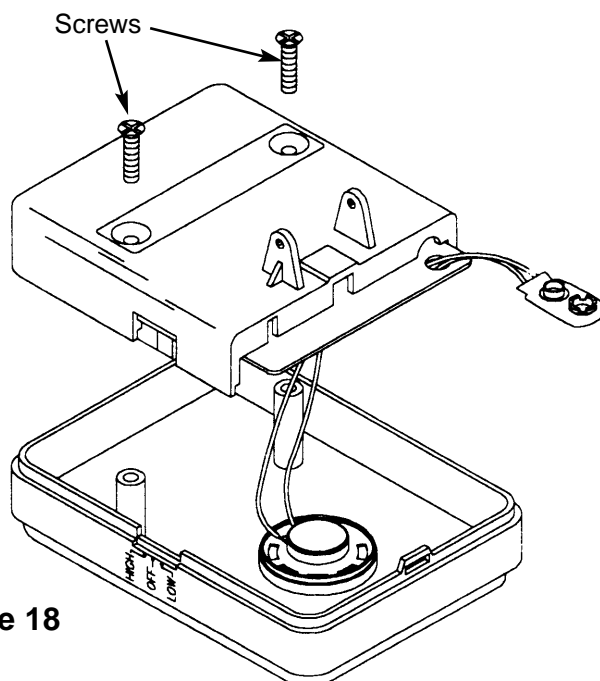


Figure 18

Step 4

Attach a 9V battery to the battery snap and place it into the case. Snap the battery cover into the back case as shown in Figure 19.

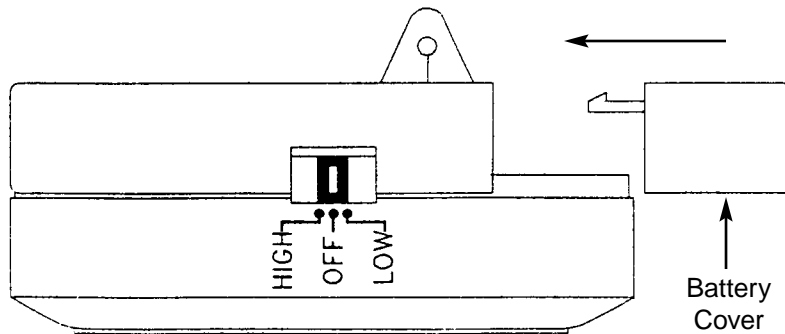


Figure 19

Step 5

Place the unit onto a table and turn it on. Move to one side of the detector so that you are out of the field of view of the detector. Walk in front of the detector and a tone will sound from the speaker. The unit is now ready for use.

Note: When the switch is in the OFF position, it disconnects the voltage to the sound generator IC only. The rest of the circuit is still operating. The battery will run down if it is left in the OFF position for long periods of time. To increase battery life, remove the battery if you intend to leave the unit in the OFF position for long periods of time.

INSTALLATION

The detector can be either placed on a flat surface or mounted onto a wall. Adjust the angle lever to the open position (see Figure 20). Align the two tabs on the bracket with the two grooves on the case. Adjust for the desired angle and move the angle lever to the lock position.

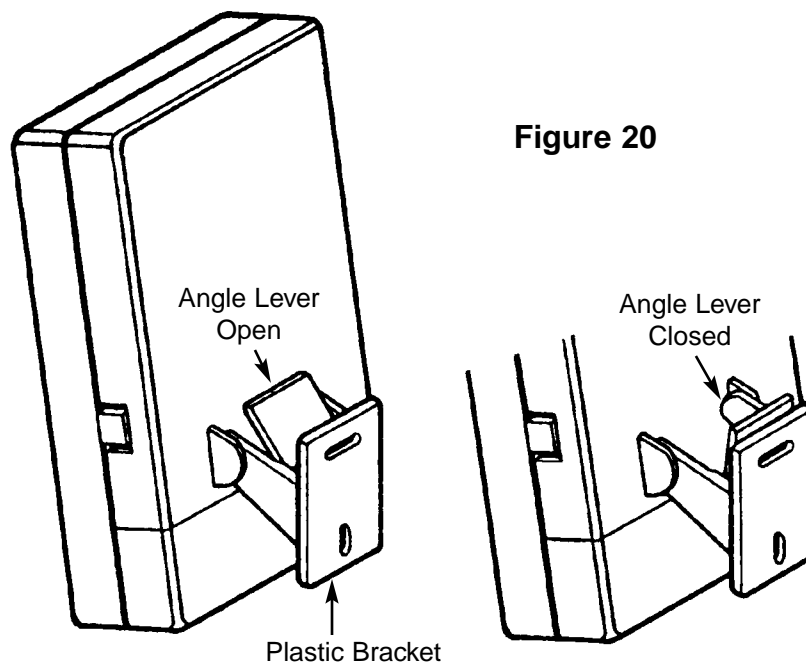


Figure 20

TROUBLESHOOTING GUIDE


The values given below are approximate.

POWER SUPPLY

1. Measure the voltage at IC3. Pin 3 = 9V, Pin 1 = 4.75 - 5.25V
 - A. Check soldering around IC3 and C6.
 - B. Check for short to GND from pins 2 and 3.
 - C. If no shorts are present, IC3 may be defective.

INFRARED DETECTOR

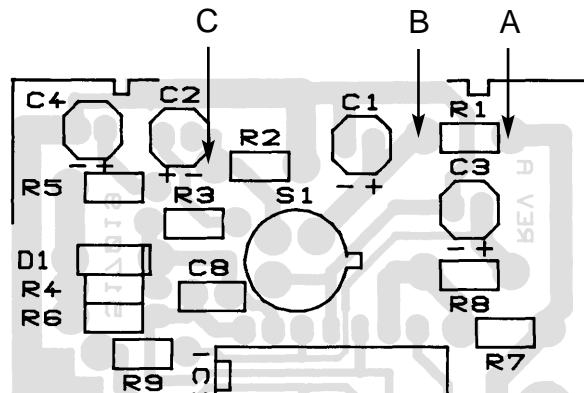2. Measure the voltages at points:
A = 5V
B = 4.25V
C = .700V
 - A. Voltage at point A incorrect:
 1. Check R1.
 2. Check for a short between point A and GND.
 - B. Voltage at point B incorrect:
 1. Check R1, C1 for correct value.
 2. Check for a short between point B and GND.
 - C. Voltage at point C incorrect:
 1. Check R2, C2 for correct value.
 2. Check for a short between point B and GND.



OPERATIONAL AMPLIFIERS

3. Measure the voltages at IC1 while the unit is at standby.

Pin	Voltage	Pin	Voltage
1	3.80V	8	---
2	---	9	1.62V
3	1.40V	10	1.60V
4	5.00V	11	---
5	1.40V	12	1.52V
6	1.60V	13	1.55V
7	---	14	1.50 - 1.60V

4. Measure the voltages at IC1 when activated.

Pin	Voltage
1	0 - 3.8V
7	0 - 3.8V
8	0 - 3.8V
14	1.5 - 3.8V

A. Incorrect voltage readings:

1. Check resistors R3 - R12 for correct value.
2. Check diode D1 polarity.
3. Check C3 and C4 polarity.
4. IC1 may be defective.

SOUND GENERATOR

Measure the voltage at the following pins on U2, as listed in the chart below.

U2 Pin	Voltage No Sound	Voltage Sound
3	0	0 - 4V
5	5V	5V
6	5V	
7	0V	.735V

A. No voltage at pin 3:

1. Check R13, R14, SW1 and C5.


B. No 5V at pin 5:

1. Check SW1 solder connection.
2. No 5V at pin 6.
3. Check C9.

C. Outputs two short tones:

1. Check C5.

Q1 Pin	Voltage No Sound	Voltage Sound
E	0	0V
B	0V	.355V
C	9V	9V

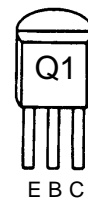


QUIZ

1. The 9V battery supplies a . . .
 - A. positive AC voltage.
 - B. DC voltage.
 - C. AC voltage.
 - D. rectified DC voltage.
2. A human's maximum thermal radiation is between . . .
 - A. 3 and 5 μ m.
 - B. 9 and 13 μ m.
 - C. 10 and 20 μ m.
 - D. 9 and 10 μ m.
3. As temperature changes, the pyroelectric crystals generate . . .
 - A. white light.
 - B. infrared light.
 - C. heat.
 - D. a voltage.
4. A wavelength is the distance between two points having . . .
 - A. opposite phases.
 - B. two different phases.
 - C. the same phase, but different voltages.
 - D. the same phase and voltage.
5. Infrared can be thought of as heat radiation because the . . .
 - A. electrical energy is transformed into heat.
 - B. radiant energy is transformed into heat.
 - C. mechanical energy is transformed into heat.
 - D. solar energy is transformed into heat.
6. What are the two inputs called in an op-amp?
 - A. non-inverting and inverting.
 - B. V_1 and V_2 .
 - C. V_{EE} and V_{CC} .
 - D. gates.
7. A high pass filter attenuates all signals . . .
 - A. between two frequencies.
 - B. below the critical frequency.
 - C. above the critical frequency.
 - D. with high amplitudes.
8. The formula for the closed loop gain is . . .
 - A. $(R_2 \times R_1)V_o$
 - B. $(R_1/R_2)V_i$
 - C. $(R_2/R_1)V_o$
 - D. $-(R_2/R_1)V_i$
9. A low pass filter attenuates all signals . . .
 - A. between two frequencies.
 - B. below the critical frequency.
 - C. above the critical frequency.
 - D. with low amplitudes.
10. A filter with a high value in Q has a . . .
 - A. wide bandwidth.
 - B. narrow bandwidth.
 - C. long bandwidth.
 - D. attenuates less frequencies.

Answers: 1. B, 2. D, 3. D, 4. D, 5. B, 6. A, 7. B, 8. D, 9. C, 10. B

SCHEMATIC DIAGRAM

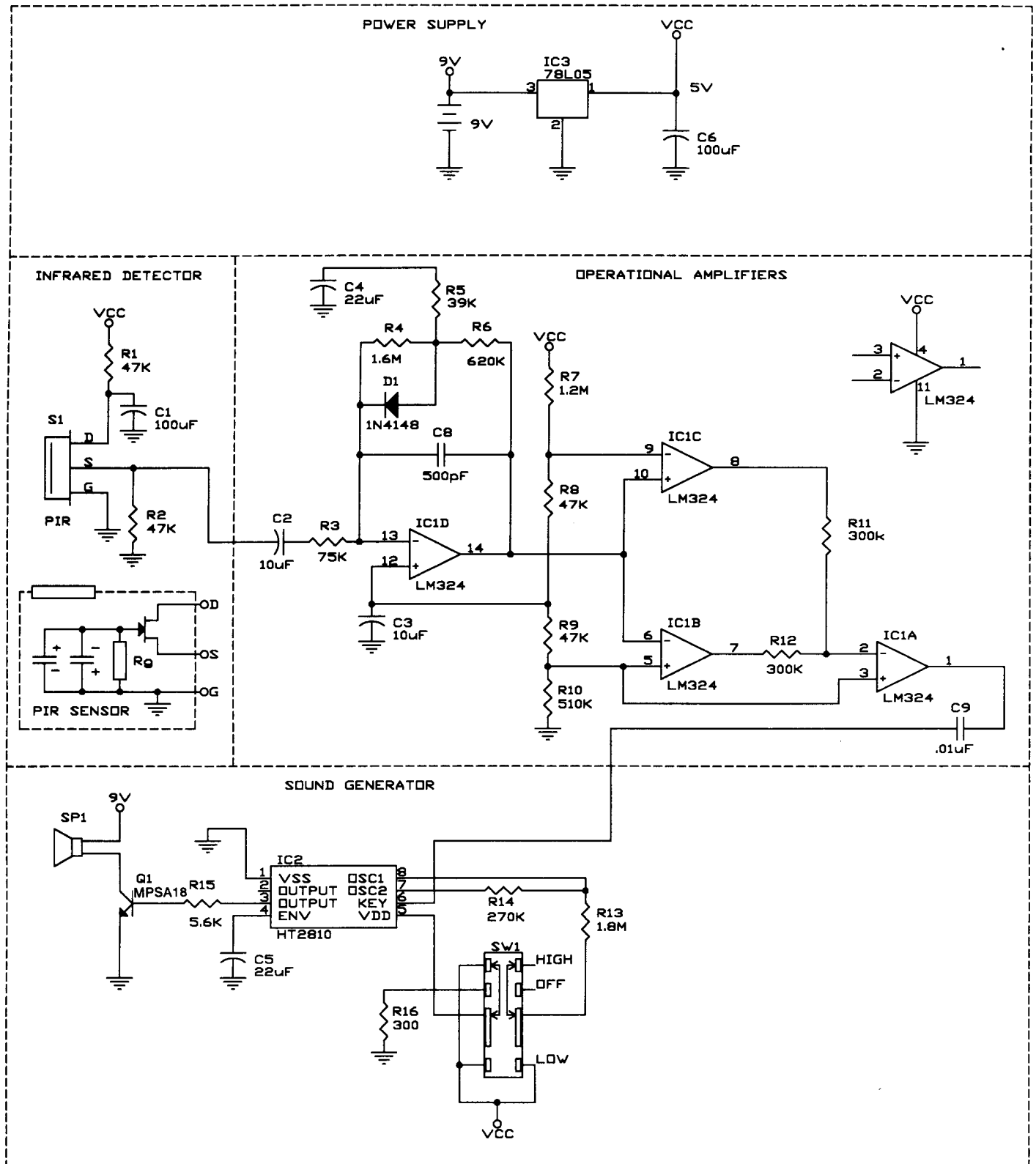

SPECIFICATIONS

Power

- 9V DC battery

Current

- Operating 60mA (average)
- Standby Typical less than 4mA

Detection

- Pyroelectric Infrared Sensor.

Detection Distance

- 30 feet max., best at 4.5' to 24'

Output Sound

- High frequency / Low frequency tone (Ding-Dong)
- 85 - 90dB peak

Operating Range

- -10 to +50°C

GLOSSARY OF TERMS

Amplify	To enlarge or increase.
Amplitude	The greatest difference above a reference, usually zero.
Analogy	Likeness or resemblance in relations of different objects.
Attenuate	To weaken or reduce.
Bandwidth	The group or number of frequencies unaffected by a filter.
Battery	A device that generates an electric current through a chemical reaction.
Capacitors	Devices that store electronic charges.
Circuit	The entire line through which electric current may pass.
Closed Loop Gain	Gain after feedback.
Comparator	An electronic device to detect voltage differences.
Critical Frequency	The frequency at which power in a filter falls to half.
Crystals	An inorganic body with plane surfaces in a geometrical form.
Current	The flow of electrons.
Detector	A device that changes signals into useful information.
Electromagnetic	A radiated wave having both electric and magnetic properties.
FET	Field Effect Transistor.
Filter	A device used to nullify certain waves without altering others.
Frequency	The repeated occurrence of anything at brief intervals.
Gain	To increase or make larger.
Gate	A device used to allow or restrict passage.
Generator	A device that transforms energy into electric power or signals.
Impedance	A device's resistance to the passage of electrical current.
Infrared Light	Rays past the red end of the visible light spectrum.
IR Detector	A device that senses the presence of infrared light.
Kit	A collection of equipment or components.
Lambda	The eleventh letter of the Greek Alphabet.

Low Pass Filter	Decreases all signals above a certain frequency and passes frequencies below that frequency.
Negative Feedback	To allow a portion of the output signal to be brought back and cancel part of the input.
Noise	A random, persistent disturbance of a signal.
Open Loop Gain	The maximum gain available without feedback.
Oscillator	A device used to vary between alternate extremes (varies from high to low).
Peak	The top of a wave or mountain.
Polarity	The division of two opposites.
Power	Electrical energy; strength, force, or might.
Pyroelectric Effect	When certain metals change temperature, they produce energy.
RC Network	An assembly of resistors and capacitors.
Reference Voltage	Level of electronic element used for providing resistance in a circuit.
Resistor	An electric element used for providing resistance in a circuit.
Response Curve	The shape of an output produced by a circuit.
Solder	An alloy (mixture) of tin and lead used in the melted state to join or repair metal parts.
Transistor	A three-terminal semiconductor device used for amplification, switching, and detection.
Valve	A mechanical device that regulates the flow of gases, liquids, or loose materials by blocking and uncovering openings.
Voltage	An electromotive force.
Wavelength	The distance in a periodic wave between 2 points of corresponding phases.\

For further information on infrared light and waves . . .

The Invisible World of the Infrared

By Jack R. White

New York: Dodd, Mead, © 1984

124 p.; ill.

Waves and Vibrations

By Brian Knapp

Danbury, CT: Grolier, © 1994

48 p.; ill.

